

Mid Semester Back Paper Examination, 2023

(Old Syllabus)

Name of the Course: B.Tech.

Semester: III

Name of the Paper: Logic Design

Paper Code: TCS-301

Time: 1.5 Hours

Maximum Marks: 50

Note: (i) All questions are compulsory

(ii) Answer any one sub question (a) OR (b)

(iii) Each sub question carries 10 marks

Q1	(10X1=10 Marks)	
(a)	(i) Convert the $(14)_{10} = ()_7$ (ii) Convert the octal number 57 to its binary representation. (iii) Perform the addition of the hexadecimal numbers 14F and 29A. (iv) Convert the decimal number 45 to its binary representation. (v) What is the hexadecimal representation of the binary number 11010111?	CO1
	OR	
(b)	(i) Minimize the following Boolean expression using a Karnaugh map: $F = (A + B).(A + C).(A + D)$ (ii) Convert the given Boolean expression to its truth table and then use a Karnaugh map to find the simplified expression: $F = AB + CD'$	
Q2	(10X1=10 Marks)	
(a)	(i) Perform the subtraction of the binary numbers 10110 and 1001 using two's complement method. (ii) Implement the given Boolean function using NAND gates only. $F = AB + B'C + BC$	CO2
	OR	
(b)	Design a combinational circuit with three input x, y, and z and three outputs A, B and C. When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.	
Q3	(10X1=10 Marks)	
(a)	Design and implement half adder and full adder using logic gates.	CO3
	OR	
(b)	Design two bit magnitude comparator using logic gates.	
Q4	(10X1=10 Marks)	
(a)	Design the combinational circuit for 2-bit Binary to Gray code converter.	CO3
	OR	
(b)	Design a 2 to 4 line decoder and draw its logic diagram.	
Q5	(10X1=10 Marks)	
(a)	Implement the expression using 4x1 multiplexer. Where c and d are control inputs $F(a, b, c, d) = \sum(0, 2, 3, 6, 8, 9, 12, 14)$	CO4
	or	

(b)	<p>A combinational circuit is defined by the following three Boolean functions. Design the circuit with a decoder and external gates.</p> $F_1 = x'y'z' + xz$ $F_2 = xy'z' + x'y$ $F_3 = x'y'z + xy$	
-----	--	--