

H

Roll No.

TEE-201

**B. TECH. (SECOND SEMESTER)
MID SEMESTER**

EXAMINATION, March, 2024

BASIC ELECTRICAL ENGINEERING


Time : 1½ Hrs.

Maximum Marks : 50

Note : (i) Answer all questions by choosing any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

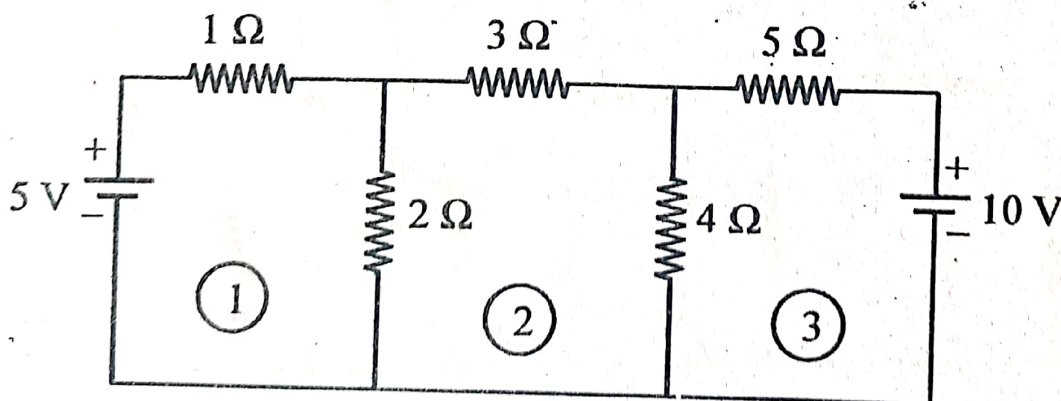1. (a) Using mesh analysis, find the value of the currents I_1 , I_2 and I_3 flowing clockwise in the first, second and third mesh respectively. (CO2)




P. T. O.

(2)


TEE-201

OR

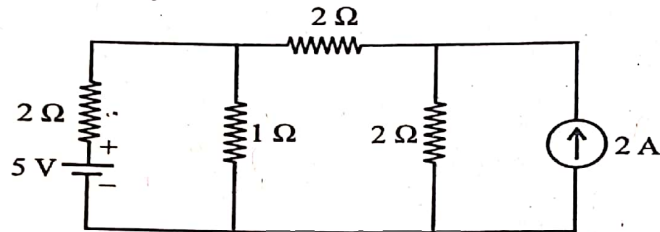- (b) Calculate current in 1 ohm using nodal analysis. (CO2)




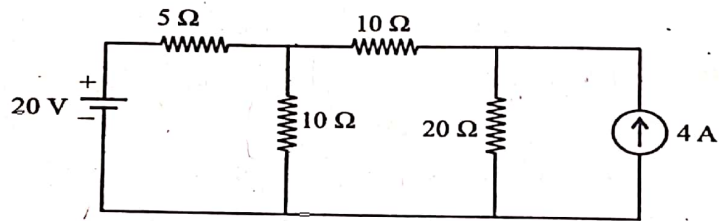2. (a) Find the current flowing through 20 Ω using the superposition theorem. (CO2)



OR

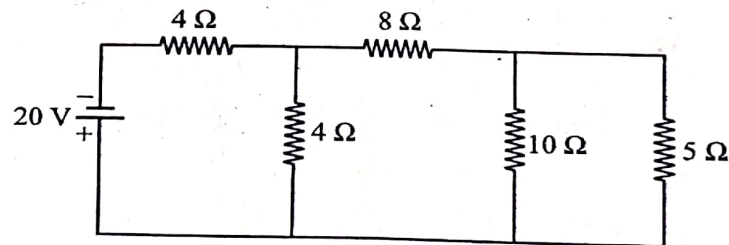- (b) Calculate the current through the load resistance (R_L) = 5 Ω using Thevenin's theorem. (CO2)



(3)

TEE-201

3. (a) (i) A capacitor of C farads is charged with q Coulomb. What is the stored energy? (CO1)
 (ii) A heating element is marked 210 V, 630 W. Find the resistance of the element when connected to a 210 V d.c. source. (CO1)

OR

- (b) (i) Explain Kirchhoff's law with example. (CO1)
 (ii) Differentiate between the following : (CO1)

- (1) Dependent and independent sources
- (2) Loop and Mesh
- (3) Unilateral and Bilateral elements
- (4) Linear and Non-linear elements


4. (a) (i) Plot a graph showing the variation of capacitive reactance with the change in the frequency of the AC source. (CO1)

P. T. O.

(4)


TEE-201

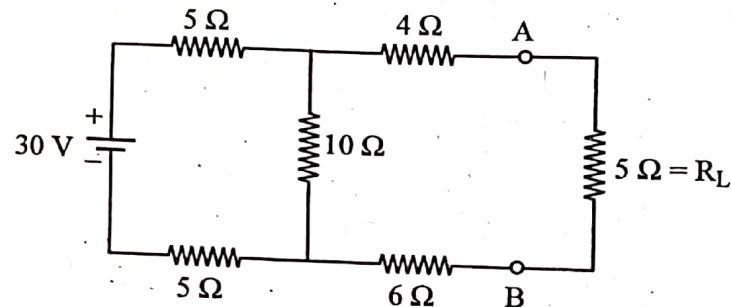- (ii) In the network shown in figure, calculate the current through the load resistor R_L by using Norton's Theorem. (CO1)



OR

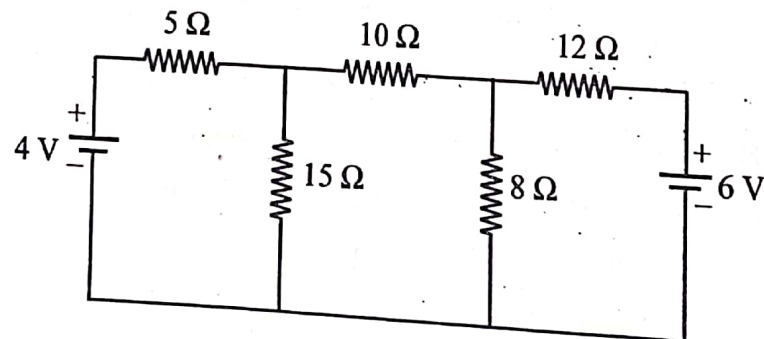- (b) By using Kirchhoff's voltage law (KVL)/Mesh analysis, find the current flowing through a 10Ω resistor. (CO1)



(5)

TEE-201

5. (a) Define the following : (CO1)
- (i) RMS and Average of AC
 - (ii) Instantaneous value of AC
 - (iii) Phase and frequency
 - (iv) Form factor and peak factor

OR

- (b) (i) An alternating current has RMS value of 50 A and frequency 60 Hz. Find the time taken to reach 50 A for the first time. (CO1)
- (ii) If the form factor of a current wave form is 2 and the peak factor is 2.5, find the average value of the current if the maximum value of the current is 500 A. (CO1)

TEE-201

3,050