

**End Term (Odd) Semester Examination December 2024**

Roll no. ....

Name of the Course and semester: B.Tech (Semester 1)

Name of the Paper: Basic electronics engineering

Paper Code: TEC 101

Time: 3 hour

Maximum Marks: 100

**Note:**

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty).
- (iv) Each sub-question carries 10 marks.

**Q1.**

(2X10=20 Marks) CO1


a.

i)  $(65)_7 = (?)_{10} = (?)_2 = (?)_{16} = (?)_8 = (?)_9$

ii) If  $(32)_X + (24)_Y = (44)_6$ , &  $(31)_X + (13)_Y = (41)_5$ , find the value of base X and base Y

b.

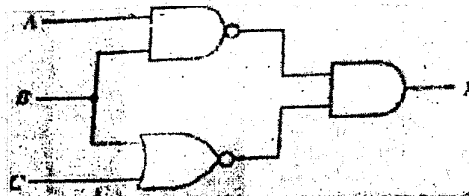i) Express the output x of given circuit in canonical SOP form.



ii) Simplify using Boolean rules  $X \oplus Y \oplus XY$

c. Minimize the following by K map and realize the minimized expression by

i) NAND gates only ii) NOR gates only

$F(A, B, C, D) = \sum m(1, 3, 4, 5, 6, 7, 9, 11, 15)$

**Q2.**

(2X10=20 Marks) CO2

a. Explain mass action law of semiconductors. If  $N_D$  and  $N_A$  are donor and acceptor impurities and  $n_i$  is the intrinsic concentration, establish the relation for minority and majority charge densities in extrinsic semiconductors.

b. Explain Avalanche breakdown and Zener breakdown mechanism. Also mention the differences among them.

c. In a Ge pn junction, donor concentration is 1000 times the acceptor concentration. If the acceptor impurity is added at the rate of 1 atom per  $10^8$  Ge atoms. Calculate built in potential at room temperature if density of Ge is  $4.4 \times 10^{26} / \text{cm}^3$  and intrinsic concentration is  $2.5 \times 10^{13} / \text{cm}^3$


**Q3.**

(2X10=20 Marks) CO3

a. With the help of circuit diagram and suitable waveforms, explain working of a Bridge rectifier. Also derive the expression for rms value of its load current.

b. What is the need of filter in a power supply? With the help of neat circuit diagram and waveforms, explain working of capacitor filter.

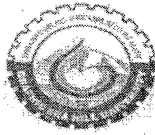c. A 100V, 50Hz ac signal is applied to the primary winding of a 5:1 step down transformer used in a half wave rectifier. If the diode used has a resistance of  $100\Omega$  and load resistance is  $1K\Omega$



**End Term (Odd) Semester Examination December 2024**

- i) Draw circuit for given data
- ii) Determine rms value of load current
- iii) Determine Output power delivered to load
- iv) Determine Rectifier efficiency

Q4.


(2X10=20 Marks) CO4

a. With the help of circuit diagram and suitable graph, explain input and output characteristics of a common base transistor.

b. Derive relation between dc current gain  $\alpha$  and  $\beta$  of a transistor.

In a common base connection, the emitter current is 10mA. Given that  $\alpha = 0.99$ , determine the collector current, base current and  $\beta$

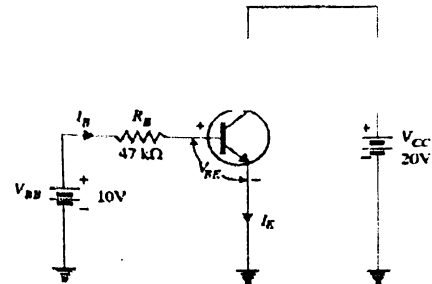c. Determine  $I_B$ ,  $I_C$ ,  $V_{CE}$  of the transistor circuit shown in Fig.  
Given  $\beta = 200$  and  $V_{BE} = 0.7V$



Q5.

(2X10=20 Marks) CO5


a.

i) List characteristics of an ideal OP-AMP

ii) Draw circuit diagram of a non-inverting amplifier using OP-AMP and derive expression for its output voltage.

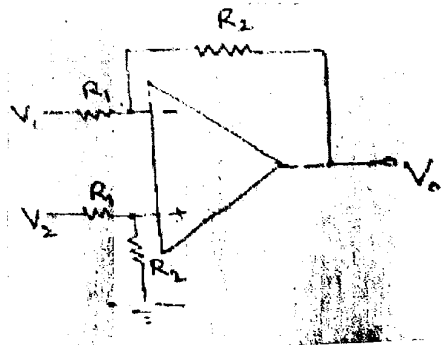b. Derive the expression for output voltage  $V_o$  for the circuit shown in figure.

Determine output voltage if  $V_1=7V$ ,  $V_2=4V$ ,  $R_1=5K\Omega$ ,  $R_2=15K\Omega$



c. Determine the  $V_x$  and output voltage  $V_o$  for the circuit shown in figure

